

ELECTRICAL TECHNOLOGY: DIGITAL

EXAMINATION NUMBER

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Time: 3 hours

200 marks


ANSWER SHEET

Attach this Answer Sheet as the last page to your Answer Book.

Use a pen for all sketches.


QUESTION 4 SWITCH AND CONTROL CIRCUITS

4.2.2

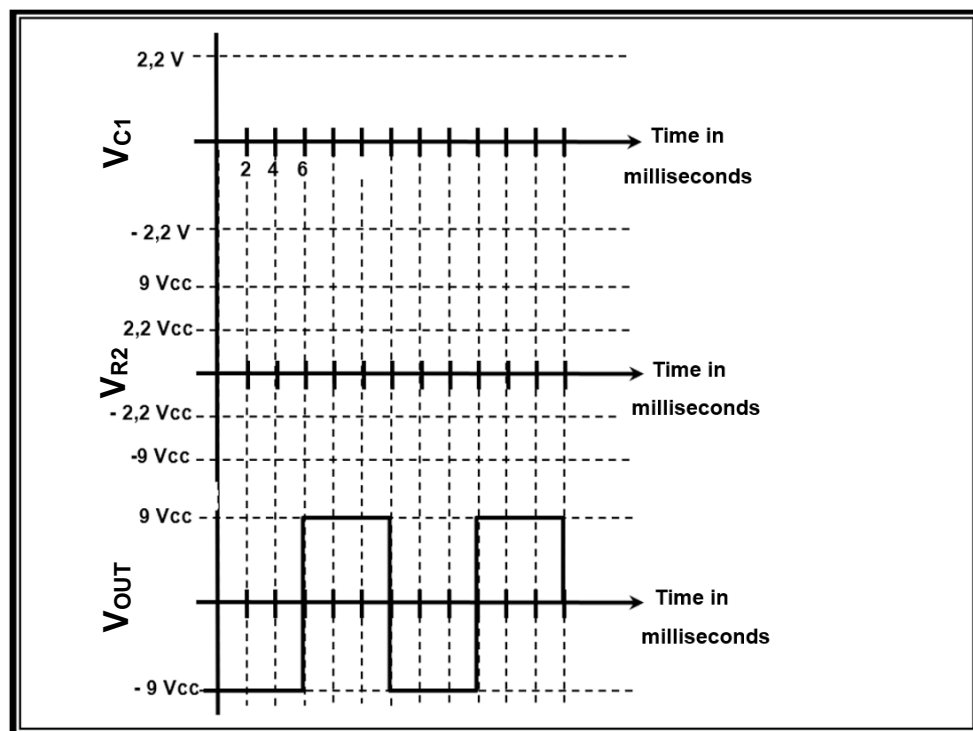

(4)


4.6.2

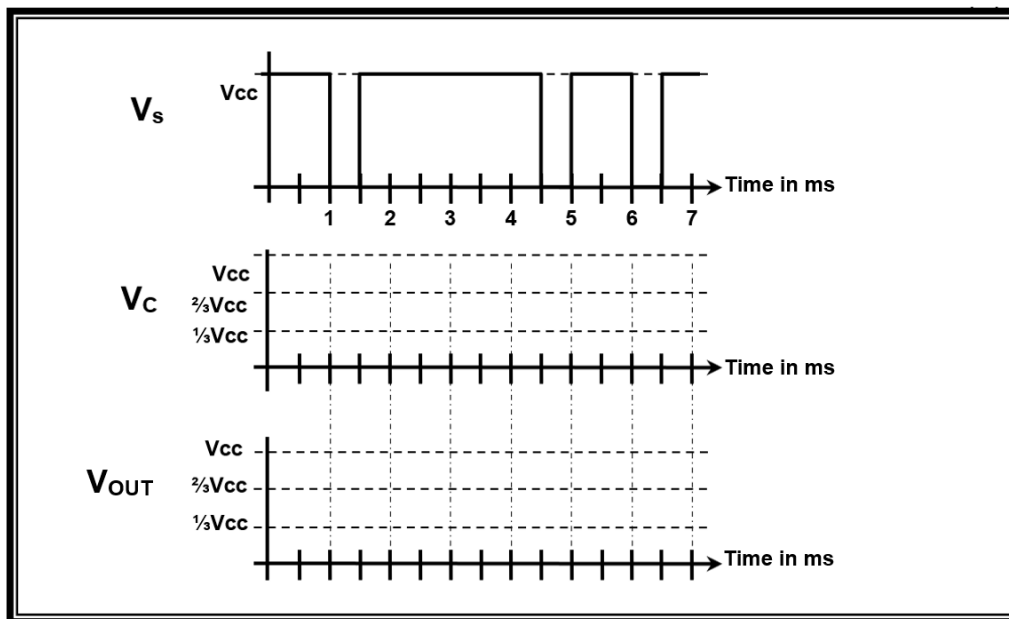

(4)

QUESTION 5 DIGITAL AND SEQUENTIAL DEVICES

5.5.1 AND 5.5.2

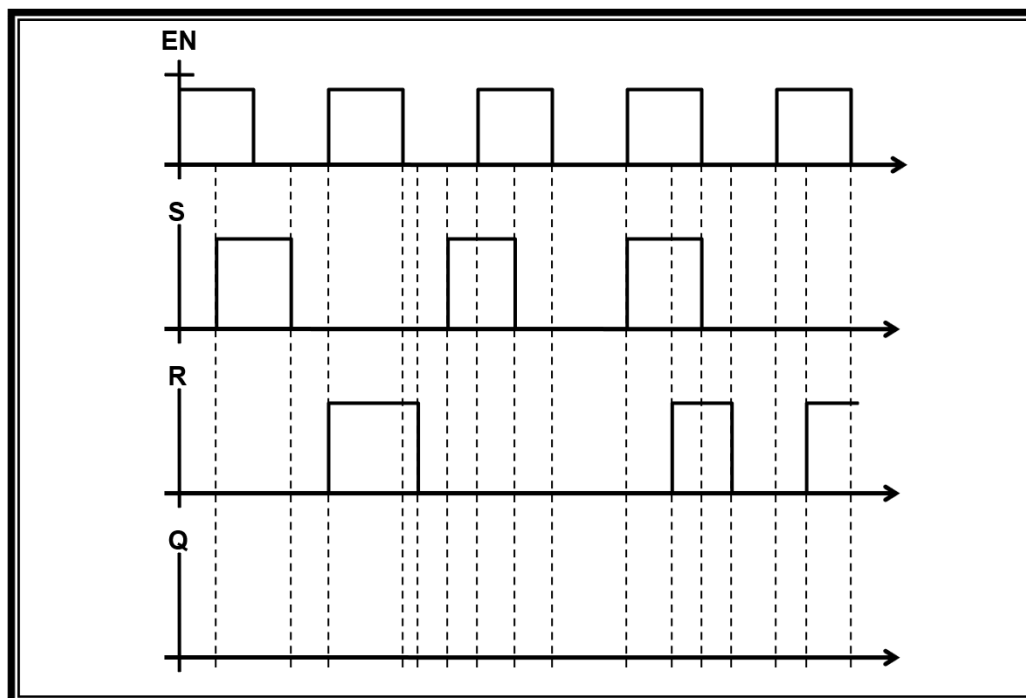

(4 + 3)